

- 6 (a) A lamp is connected in parallel to a resistor of resistance R . These are connected in series to a resistor of resistance $3.0\ \Omega$ and a power supply of electromotive force (e.m.f.) 6.0 V and of negligible internal resistance, as shown in Fig. 6.1.

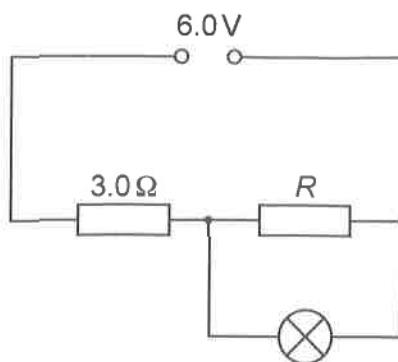


Fig. 6.1

The current in the lamp is 0.30 A and its resistance is $5.0\ \Omega$.

- (i) Determine the resistance R . Show your working.

$$R = \dots\dots\dots \Omega \text{ [3]}$$

- (ii) The power supply transfers 120 J of energy to the circuit.

Determine the energy transferred in the lamp. Show your working.

$$\text{energy} = \dots\dots\dots \text{ J [3]}$$





- (iii) Explain why the current in the filament lamp is greatest when the current is first switched on.

.....

.....

.....

..... [2]

- (b) Two lengths of resistance wire, X and Y, made from different materials, are connected in series to a power supply, as shown in Fig. 6.2.

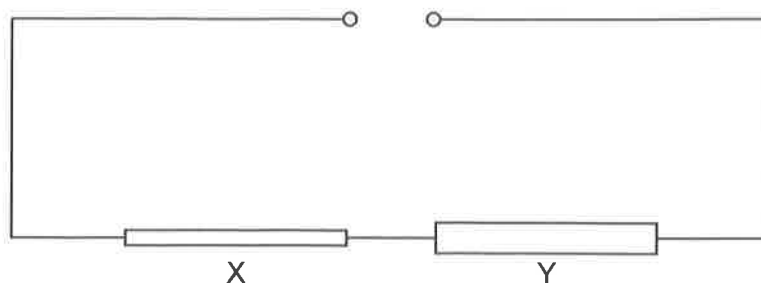


Fig. 6.2

Wire X has half the radius of wire Y.

The drift velocity of the electrons in wire X is three times the drift velocity of the electrons in wire Y.

Determine the ratio

$$\frac{\text{number density of charge carriers in Y}}{\text{number density of charge carriers in X}}$$

Show your working.

ratio = [3]

[Total: 11]

