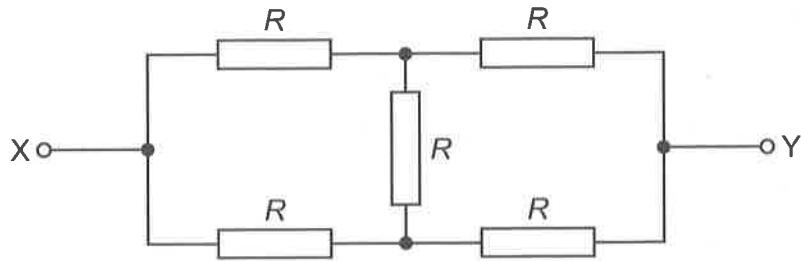


**23** The diagram shows a network of resistors each of resistance  $R$ .



What is the resistance of this network, measured between the terminals  $X$  and  $Y$ ?

**A**  $R$

**B**  $1.5R$

**C**  $3R$

**D**  $4.5R$

**24** The diagram shows part of a circuit