

- 22** An electron travels around the circuit shown in the diagram. The cell has negligible internal resistance.

At which point in the circuit does the electron have its maximum electrical potential energy?

