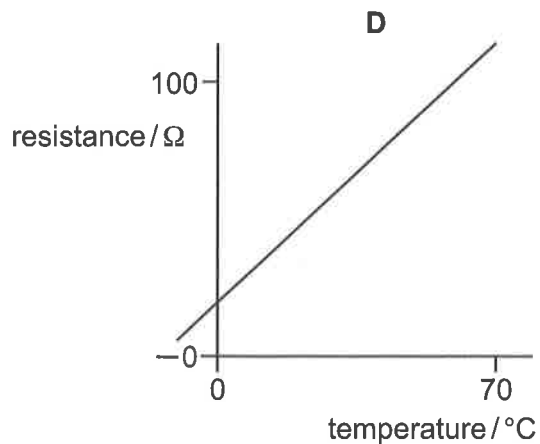
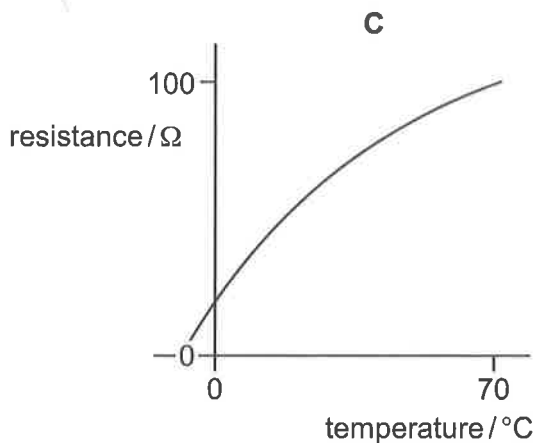
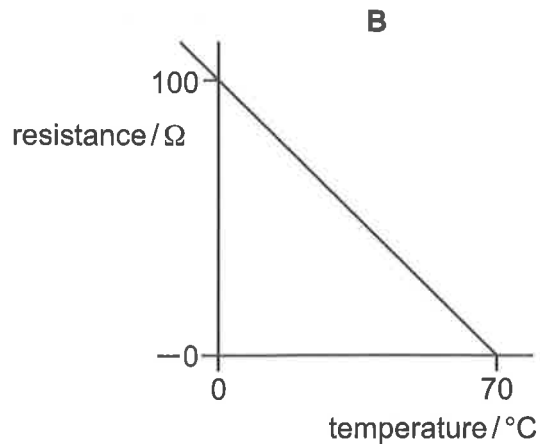
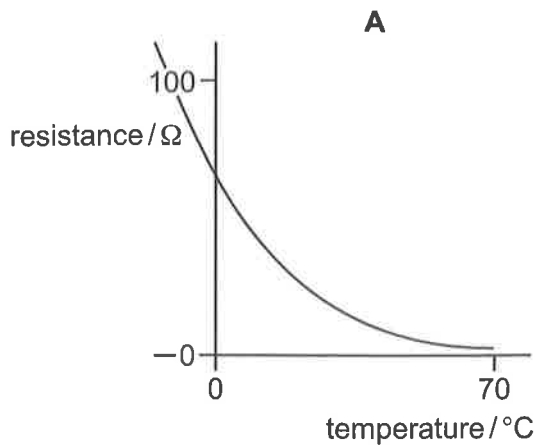


18 Which graph depicts the temperature characteristic of a thermistor?



19 A power supply is connected in series with a $26.8\ \Omega$ resistor and a switch