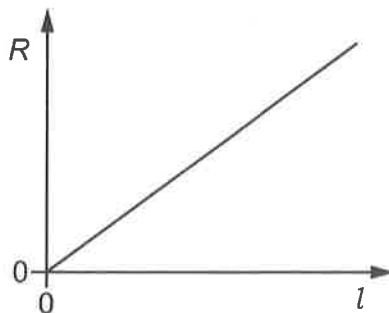
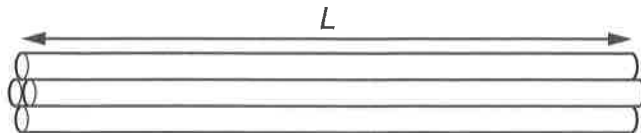


- 21 The resistance R of a length l of a uniform, cylindrical wire is measured for different values of l . The graph of R against l has a gradient G .



Four lengths of this wire are assembled into a composite wire as shown.



What is the resistance of the composite wire between the two ends?

- A $\frac{GL}{16}$ B $\frac{GL}{4}$ C $4GL$ D $16GL$

