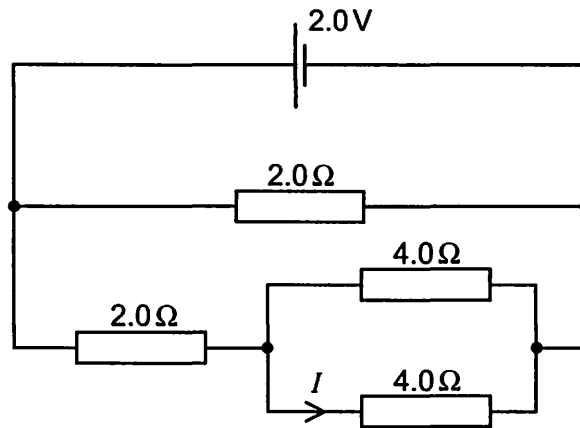


- 24 A cell of e.m.f.  $2.0\text{ V}$  and negligible internal resistance is connected to a network of resistors as shown.



What is the current  $I$ ?

- A  $0.25\text{ A}$       B  $0.33\text{ A}$       C  $0.50\text{ A}$       D  $1.5\text{ A}$