

- 20 A battery with electromotive force (e.m.f.) E and negligible internal resistance is connected to a lamp and resistors.

Which circuit provides a variable potential difference from 0 to E across the lamp?

