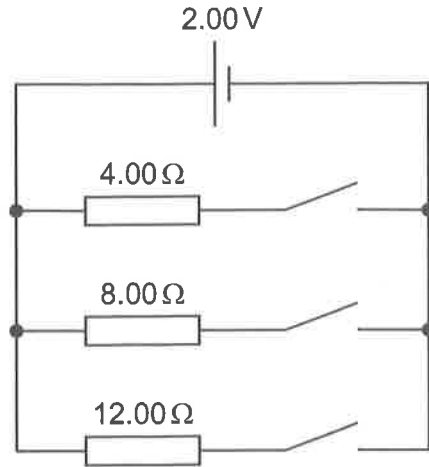


**23** The circuit shown contains a cell with negligible internal resistance.



What is the current in the cell when every switch is closed?

**A** 0.0625 A

**B** 0.0833 A

**C** 0.125 A

**D** 0.917 A

**24** A stationary electron is at a point where there is a gravitational field and a magnetic field. Both