

26 A resistor of resistance R has a power rating P when the current in the resistor is I .

What is the resistance of a resistor that has the power rating P for a current of $2I$?

A $\frac{1}{4}R$

B $\frac{1}{2}R$

C $2R$

D $4R$