

- 3 (a) An electrical component C has an  $I$ - $V$  characteristic as shown in Fig. 3.1.

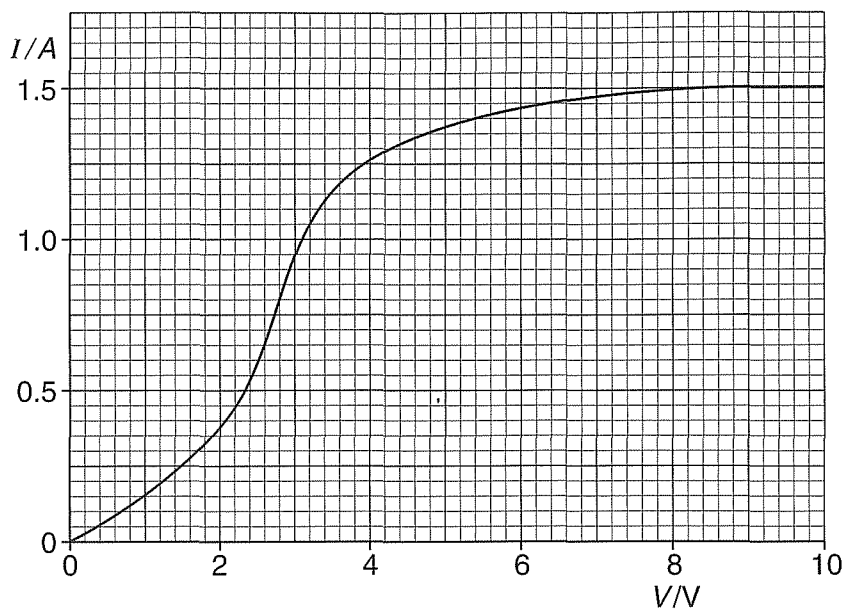


Fig. 3.1

- (i) Calculate the resistance of component C when a p.d. of 6.0 V is applied across it.

resistance = .....  $\Omega$  [1]

- (ii) Deduce the minimum value of the resistance of component C over the range 0 – 10 V.

resistance = .....  $\Omega$  [2]

- (b) Component C is then connected into a circuit with a supply of internal resistance  $0.80\ \Omega$  and a resistor of constant resistance  $5.0\ \Omega$ , as shown in Fig. 3.2.

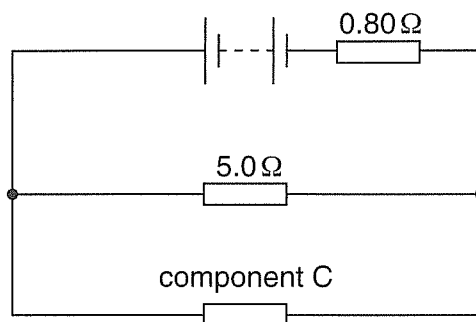


Fig. 3.2

The current through the  $5.0\ \Omega$  resistor is found to be  $0.85\ \text{A}$ .

Calculate

- (i) the p.d. across component C,

p.d. = ..... V [2]

- (ii) the total current from the supply,

current = ..... A [2]

- (iii) the e.m.f. of the supply,

e.m.f. = ..... V [2]

- (iv) the energy supplied to component C in 20 minutes.

energy = ..... J [3]