

- 5 Fig. 5.1 shows a circuit containing six resistors connected to a 12V battery with negligible internal resistance.

Q is a point in the circuit.

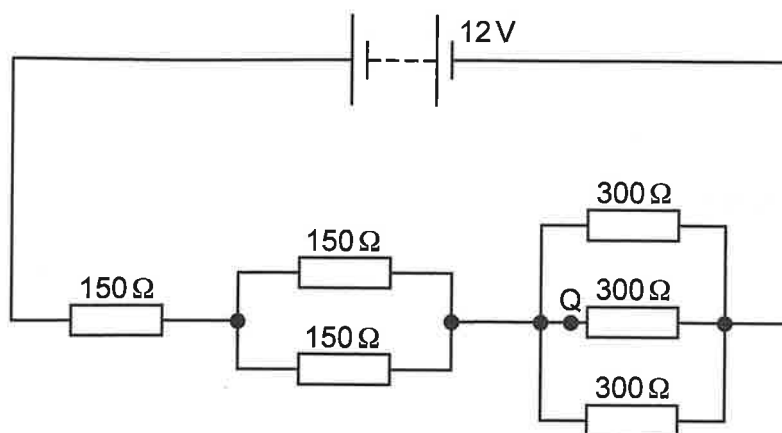


Fig. 5.1

- (a) Calculate the total resistance of the circuit.

resistance = Ω [3]

- (b) Calculate the current in the cell.

current in cell = A [1]

- (c) Calculate the current at point Q.

current at Q = A [1]

[Total: 5]

