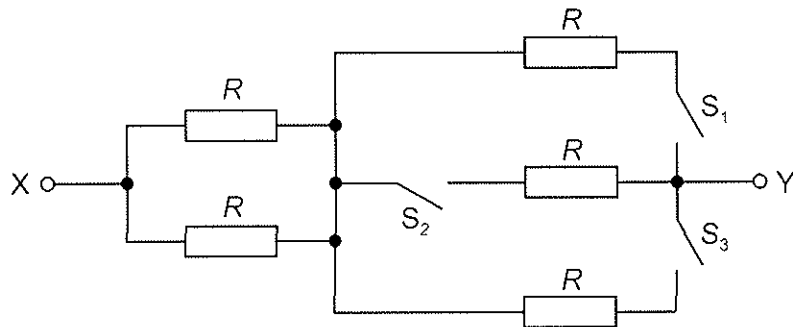


- 31 A network is constructed using five resistors, each of resistance  $R$ , and three switches  $S_1$ ,  $S_2$  and  $S_3$ .



Which switch combination will give rise to the maximum total resistance between points X and Y?

	$S_1$	$S_2$	$S_3$
<b>A</b>	closed	closed	closed
<b>B</b>	closed	open	closed
<b>C</b>	open	closed	closed
<b>D</b>	open	closed	open

