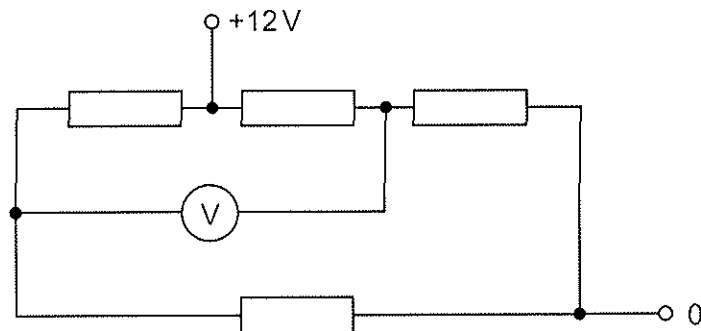


- 30 In the circuit shown, all the resistors have the same resistance. The resistance of the voltmeter is infinite.



The potential difference between the input terminals is 12V.

What is the reading on the voltmeter?

- A zero                      B 4V                      C 6V                      D 8V