

34 The mean power dissipated in a resistor of resistance 10Ω by a sinusoidal alternating current is 160 W .

What is the r.m.s. value of the current?

A 2.8 A

B 4.0 A

C 5.7 A

D 16 A