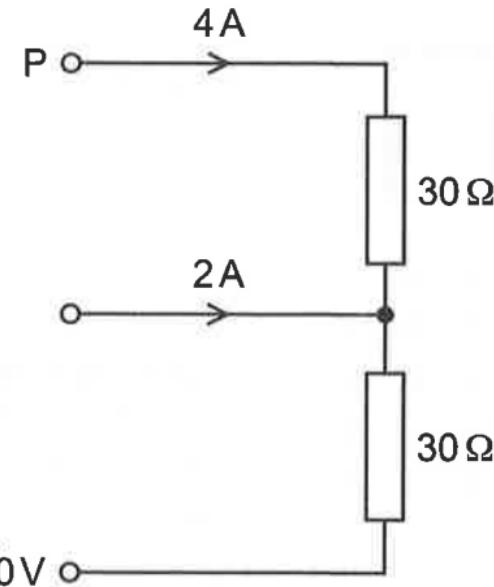


- 22 The diagram shows part of an electrical circuit. The currents in two of the wires of the circuit are shown.



What is the potential at P?

A 120 V

B 180 V

C 240 V

D 300 V