

- 4 (a) On Fig. 4.1, sketch a line to show the  $I$ – $V$  characteristic of
- (i) a metallic conductor at a constant temperature and label the line M,
  - (ii) a filament lamp and label the line F.

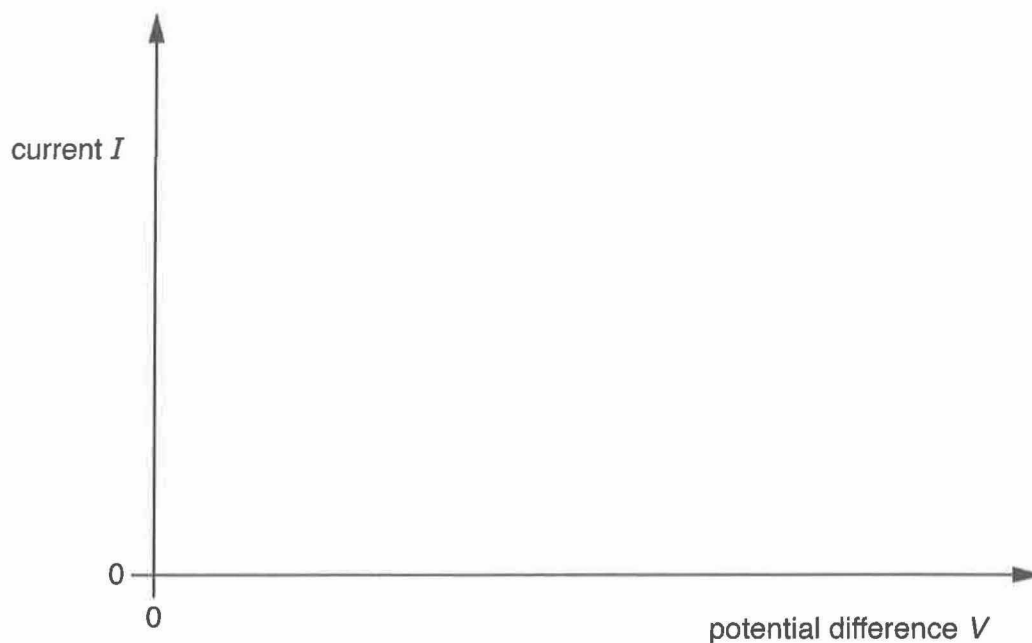


Fig. 4.1

[2]

- (b) On Fig. 4.2, sketch a graph showing how the resistance of a thermistor varies with temperature.

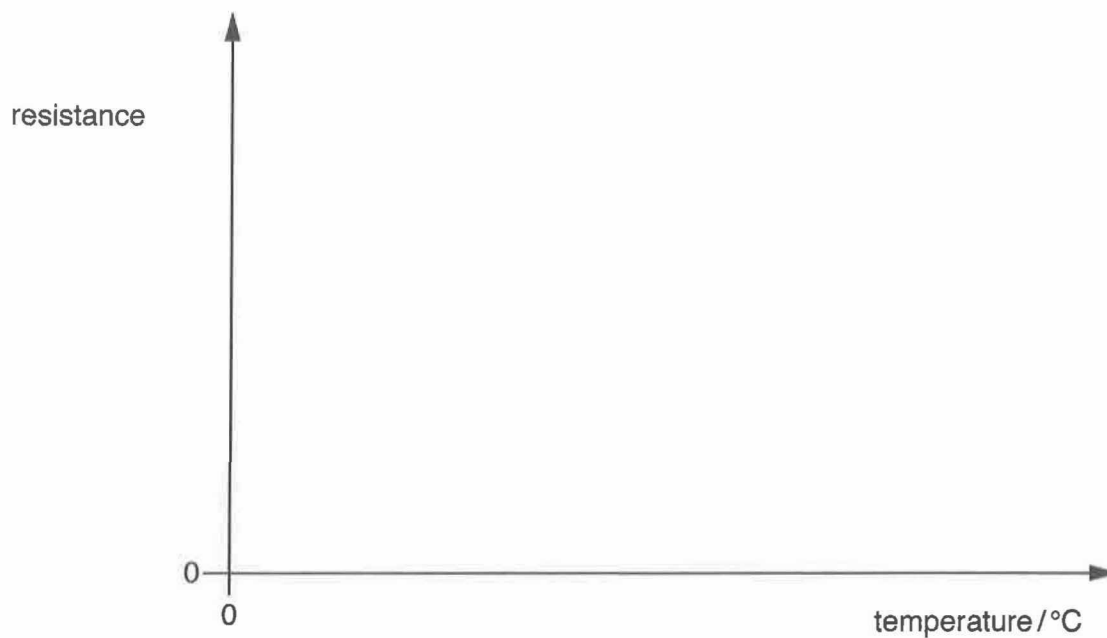


Fig. 4.2

[1]



(c) The filament of an electric lamp, suitable for use with 110V mains, has an area of cross-section of  $7.9 \times 10^{-12} \text{ m}^2$ , a length of 32mm and a resistivity of  $5.5 \times 10^{-8} \Omega \text{ m}$  at room temperature.

(i) Calculate the resistance of the lamp at room temperature.

resistance = .....  $\Omega$  [3]

(ii) Draw a circuit diagram to show how six of these lamps can be connected to a 220V mains supply so that all of the lamps shine with normal brightness.

[2]

[Total: 8]

