

35 A sinusoidal alternating current of r.m.s. value I is passed through a resistor of resistance R .

Which graph shows how the power P dissipated in the resistor varies with time t ?

