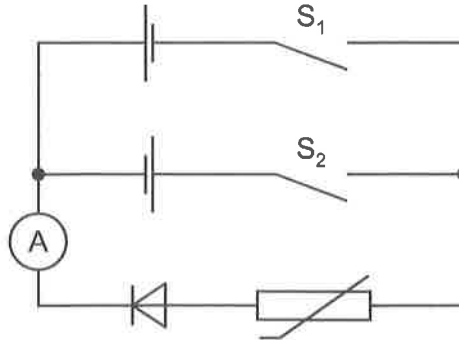


- 23** Two electrical components are connected in series with an ammeter in the circuit shown. The cells are identical.



Which circuit arrangement and level of temperature gives the largest reading on the ammeter?

	S_1	S_2	temperature
A	closed	open	high
B	closed	open	low
C	open	closed	high
D	open	closed	low

