

21 What is the rate of flow of electrons in a component in which the current is 20.0 mA?

A 20 C m s^{-1}

B 20 mC s^{-1}

C $1.25 \times 10^{17} \text{ s}^{-1}$

D $1.25 \times 10^{20} \text{ s}^{-1}$

22 Two 12 V power supplies P and Q are connected to two heaters of the same constant resistance...