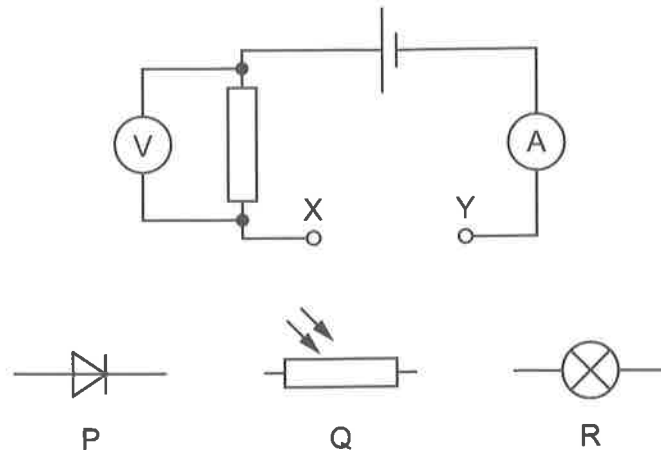


- 22** A circuit has connectors at X and at Y that enable one of the three components, P, Q and R, to be connected into the circuit.



Which components, when connected separately, give meter readings that change when the component connections to X and Y are reversed?

- A** P only **B** R only **C** P and Q **D** Q and R

- 23** A stationary negative charge at X in an electric field experiences an electric force, as shown.