

22 Four resistors, with resistances as shown, are connected in series and parallel combinations.

Which combination has the **lowest** total resistance?

