

- 9 (a) By reference to heating effect, explain what is meant by the *root-mean-square* (r.m.s.) value of an alternating current.

.....
.....
.....

[2]

- (b) An electric heater has a resistance of 38Ω at its working temperature. The variation with time t of the supply voltage V connected between the terminals of the heater is given by

$$V = 240 \sin 377 t,$$

where V is measured in volts and t is in seconds.

Determine

- (i) the frequency f of the supply voltage,

$$f = \dots \text{Hz} [2]$$

- (ii) the power dissipation of the heater.

$$\text{power} = \dots \text{W} [3]$$



- (c) The voltage of the supply in (b) is to be stepped down to 12V r.m.s. using a transformer, as illustrated in Fig. 9.1.

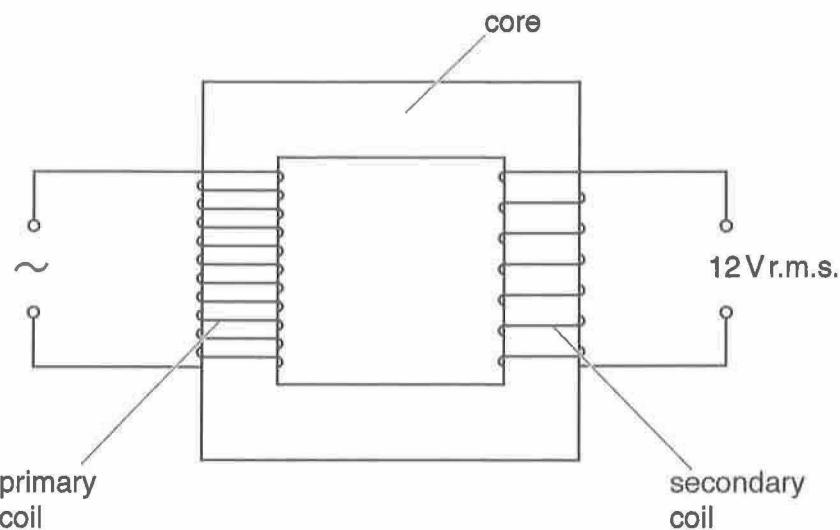


Fig. 9.1

- (i) 1. State Faraday's law of electromagnetic induction.

.....
.....
.....
.....

[2]

2. Use Faraday's law to explain why an alternating current in the primary coil gives rise to an **alternating e.m.f.** in the secondary coil.

.....
.....
.....
.....
.....
.....

[4]

- (II) The primary coil is wound with 5000 turns. The transformer is assumed to be ideal.

1. Explain what is meant by an *ideal* transformer.

..... [1]

2. Calculate the number N of turns on the secondary coil.

$$N = \dots \quad [2]$$

- (III) In practice, the core of some transformers is made of laminated soft iron.

1. State two reasons why soft iron, which is easily magnetised and demagnetised, is used as the core.

.....
.....
..... [2]

2. Explain how the lamination of the core reduces energy losses.

.....
.....
..... [2]

