



- 3 The variation with potential difference V of current I for a semiconductor diode is shown in Fig. 3.1.

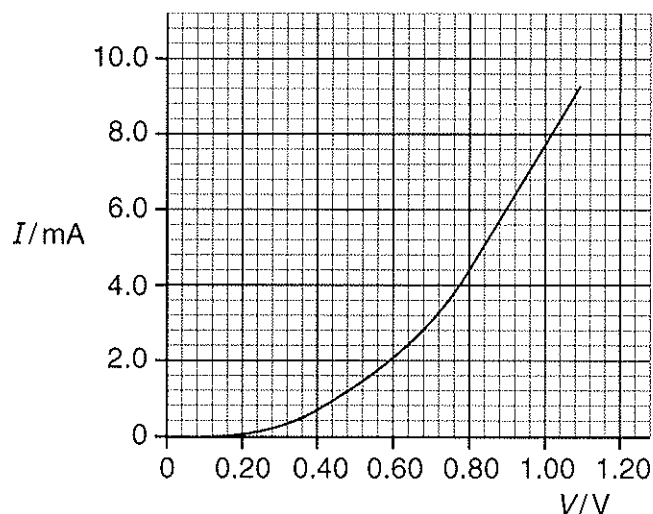


Fig. 3.1

- (a) (i) Describe the main features of Fig. 3.1 that show the characteristics of the diode in terms of current, voltage and resistance.

.....

.....

.....

.....

.....

..... [4]

- (ii) Use Fig. 3.1 to determine the resistance of the diode at 0.80V.

resistance = Ω [2]



- (b) In an attempt to obtain the graph of Fig. 3.1 for the diode, a student sets up a circuit as shown in Fig. 3.2.

For
Examiner's
Use

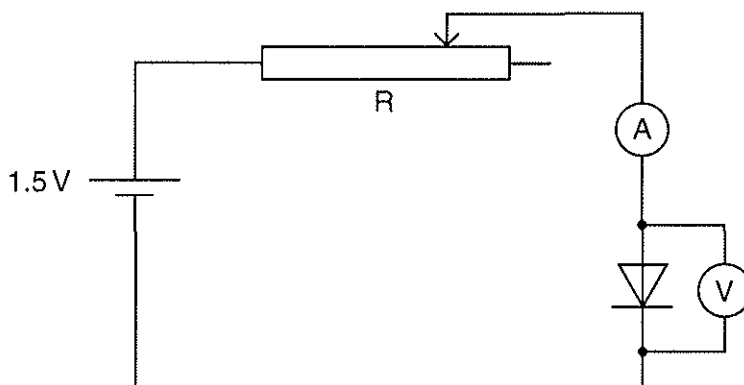


Fig. 3.2

The cell has an e.m.f. of 1.5V and negligible internal resistance. The resistor R has a resistance that can be varied between zero and 100Ω .

State and explain why the circuit shown in Fig. 3.2 is inappropriate for determining the graph of Fig. 3.1.

.....

 [2]

- (c) (i) In the space below draw a circuit diagram, using the same components as shown in Fig. 3.2, from which the graph of Fig. 3.1 may be determined.

[1]

- (ii) Explain why this circuit is appropriate for determining the graph of Fig. 3.1.

.....

 [1]

