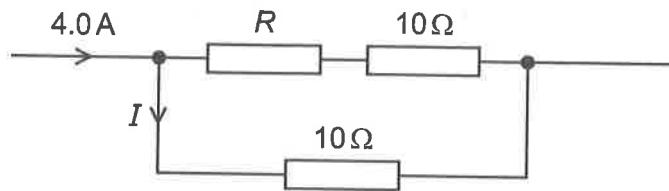


- 24 In the part-circuit shown, a current I and a resistor of resistance R are labelled.



Which row shows a possible combination for the values of R and I ?

	R/Ω	I/A
A	0	4.0
B	10	3.5
C	20	3.0
D	30	2.5

