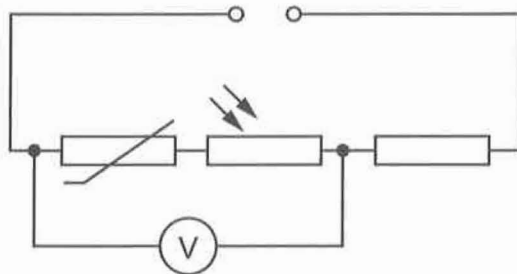


- 28** A thermistor, an LDR and a fixed resistor are connected in series to a power supply. A voltmeter is placed across the thermistor-LDR combination. The resistance of the thermistor decreases with temperature.



Which conditions of brightness and temperature will produce the smallest reading on the voltmeter?

	temperature	brightness
A	high	high
B	high	low
C	low	high
D	low	low