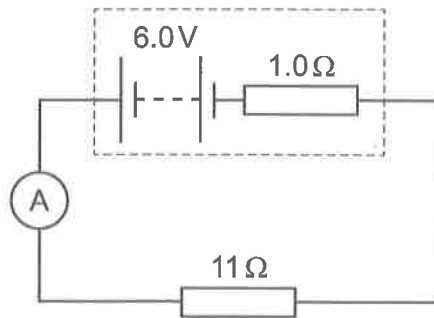


- 20 The diagram shows a battery of electromotive force (e.m.f.) 6.0 V and internal resistance $1.0\ \Omega$ connected in series with an ammeter and a resistor of resistance $11\ \Omega$.



A second identical battery is added in series with the first to give a total e.m.f. of 12.0 V .

What will be the change of the reading on the ammeter?

- A no change
- B it increases by a factor less than 2
- C it doubles
- D it increases by a factor more than 2

- 21 Two cylindrical carbon resistors P and Q connected in series have a combined resistance of