

- 37 In the diagrams below, the symbols + + + and - - - represent the majority carriers in the p-type and n-type sides of a p-n junction.

Which pair of diagrams illustrates how a p-n junction acts as a rectifier?

