

Section A

Answer **all** the questions in this section.

- 1 A cell with an internal resistance r is connected to a resistor, as shown in Fig. 1.1.

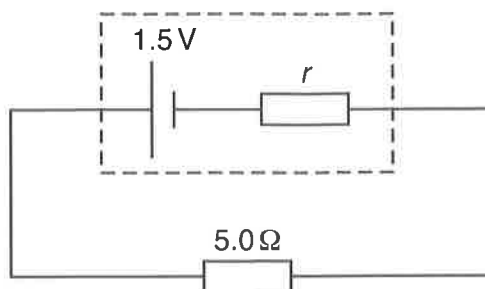


Fig. 1.1

The cell has an electromotive force (e.m.f.) of 1.5 V and a terminal potential difference of 1.2 V.

The resistor has a resistance of 5.0Ω .

- (a) Calculate the internal resistance of the cell.

internal resistance = Ω [2]

- (b) A second identical resistor is connected in parallel with the first resistor.

- (i) Calculate the resistance of the two resistors in parallel.

resistance = Ω [1]

- (ii) Explain what happens to the terminal potential difference of the cell when the second resistor is connected in parallel with the first resistor.

.....

.....

.....

..... [2]

[Total: 5]

