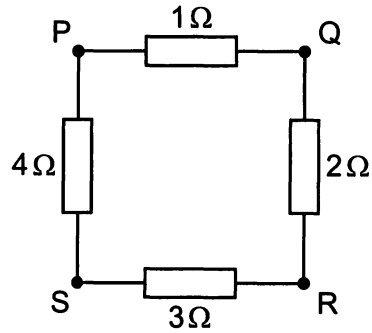


25 Four resistors are connected as shown.



Between which points is the resistance of the combination a maximum?

- A** P and Q **B** Q and S **C** R and S **D** S and P