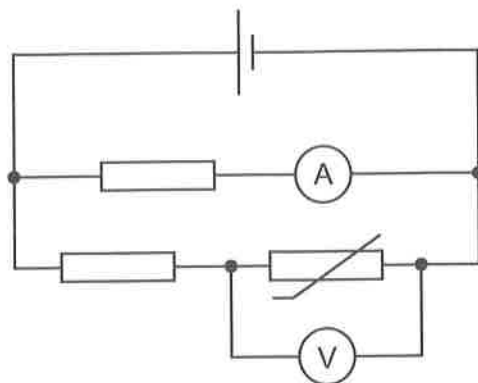


- 19 A student connects an electric circuit to investigate the changes in current and potential difference for a negative temperature coefficient (NTC) thermistor.



The cell has negligible internal resistance.

Which change occurs in the readings on the meters as the thermistor is heated?

	reading on voltmeter	reading on ammeter
A	decrease	no change
B	decrease	increase
C	increase	decrease
D	increase	no change

