

- 27 The ideal diodes shown have zero resistance in the forward direction and infinite resistance in the reverse.

In which arrangement is the potential at **X** equal to 8 V?

