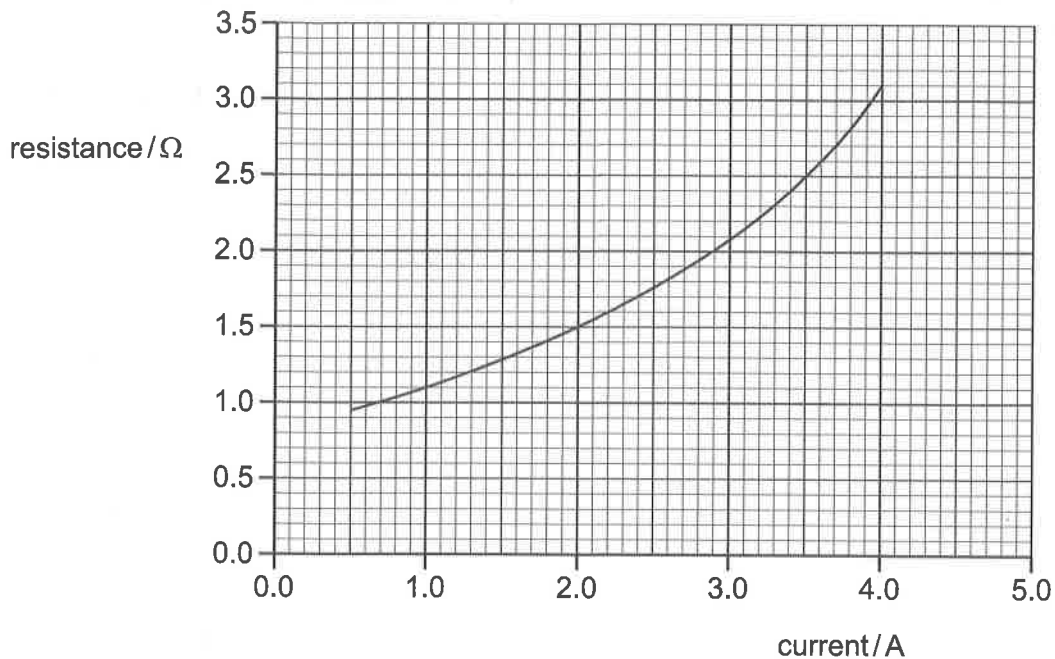


**22** The variation with current of the resistance of a lamp is shown.



What is the power of the lamp when the current is 3.4 A?

**A** 1.4 W

**B** 4.8 W

**C** 8.2 W

**D** 28 W

**23** The diagram shows a potentiometer circuit