

- 23** A semiconductor diode has a constant current in it when the potential difference (p.d.) across it is at least 2.0 V. Below this p.d. the diode is non-conducting. This diode is connected in parallel with a resistor of resistance  $4.0\ \Omega$ .

Which graph shows how the total current varies with potential difference  $V$  across the parallel arrangement?

