

- 6 A thermistor of resistance R , a fixed resistor and a cell are connected in series in a circuit. A voltmeter is connected in parallel across the resistor, as shown in Fig. 6.1.

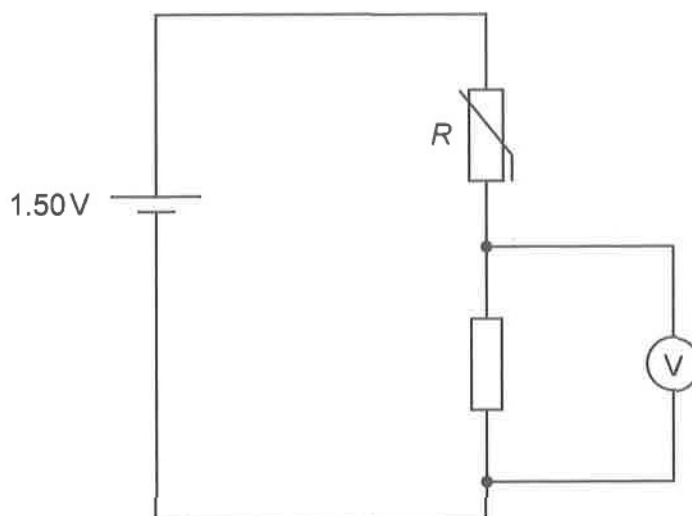


Fig. 6.1

The cell has an e.m.f. of 1.50V and negligible internal resistance.

The variation with temperature θ of the resistance R of the thermistor is shown in Fig. 6.2.

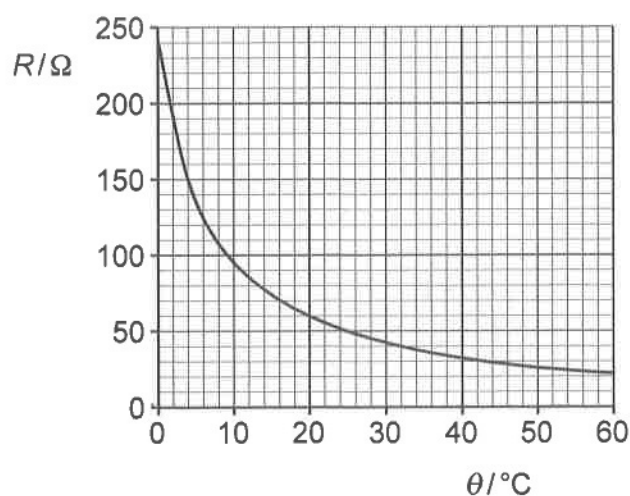


Fig. 6.2



- (a) When the thermistor is at a temperature of 20°C , the reading on the voltmeter is 0.43 V .

Show that the resistance of the fixed resistor is $24\ \Omega$.

[3]

- (b) The thermistor and resistor are then connected in parallel with the 1.50 V cell. The temperature of the thermistor is changed to 32°C .

Determine the current in the cell.

current = A [3]

[Total: 6]

