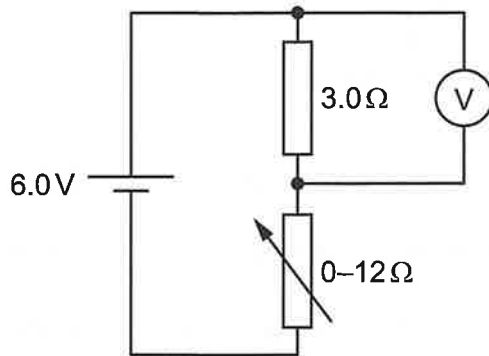


- 21 A  $3.0\ \Omega$  resistor is placed in a potential divider circuit with a  $0\text{--}12\ \Omega$  variable resistor and a  $6.0\ \text{V}$  supply. A voltmeter is attached across the  $3.0\ \Omega$  resistor.



The resistance of the variable resistor is increased from  $0\ \Omega$  to  $12\ \Omega$ .

What happens to the reading on the voltmeter during this change?

- A It decreases to  $1.2\ \text{V}$ .
- B It decreases to  $1.5\ \text{V}$ .
- C It increases to  $4.5\ \text{V}$ .
- D It increases to  $4.8\ \text{V}$ .