

24 Which combination of 12Ω resistors will give an overall resistance of 42Ω ?

- A** two in series connected to two in parallel
- B** two in series connected to three in parallel
- C** three in series connected to two in parallel
- D** three in series connected to three in parallel