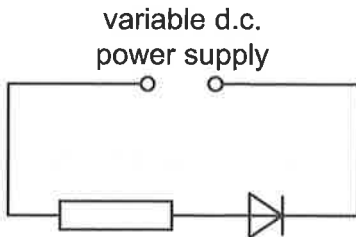


- 19 An ideal semiconductor diode and a resistor at constant temperature are connected in series with a variable d.c. power supply, as shown.



Which graph shows the variation of the current I in the circuit with potential difference V between the terminals of the power supply?

