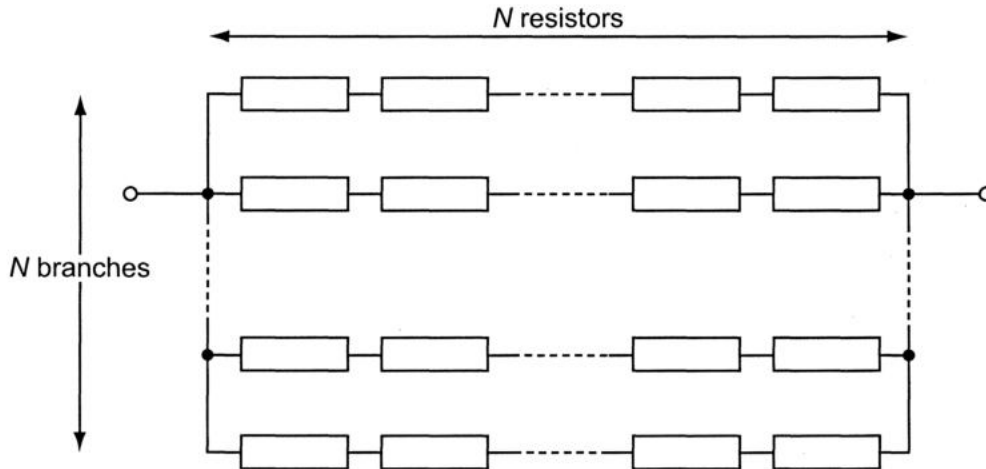


- 28 An array of resistors, each of resistance R , consists of N parallel branches. Each branch contains N resistors connected in series.



What is the total resistance of the array?

A $\frac{1}{RN}$

B $\frac{R}{N}$

C R

D NR