

- 25** A circuit is needed which switches on a warning lamp when the temperature of a thermistor is too high.

Which circuit is suitable?

