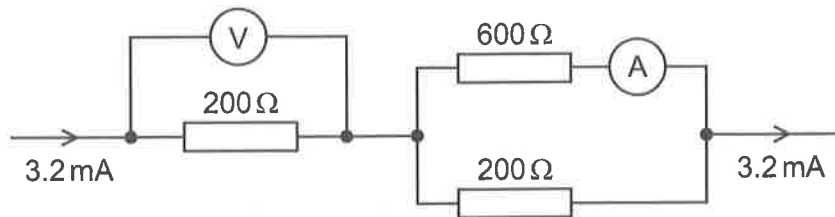


24 The diagram shows part of a circuit.



What are the readings on the voltmeter and on the ammeter?

	reading on voltmeter / V	reading on ammeter / mA
A	0.64	0.80
B	0.64	2.4
C	6.4	0.80
D	6.4	2.4

