

- 3 A battery B, a variable resistor R and a uniform resistance wire PQ are connected in series, as shown in Fig. 3.1.

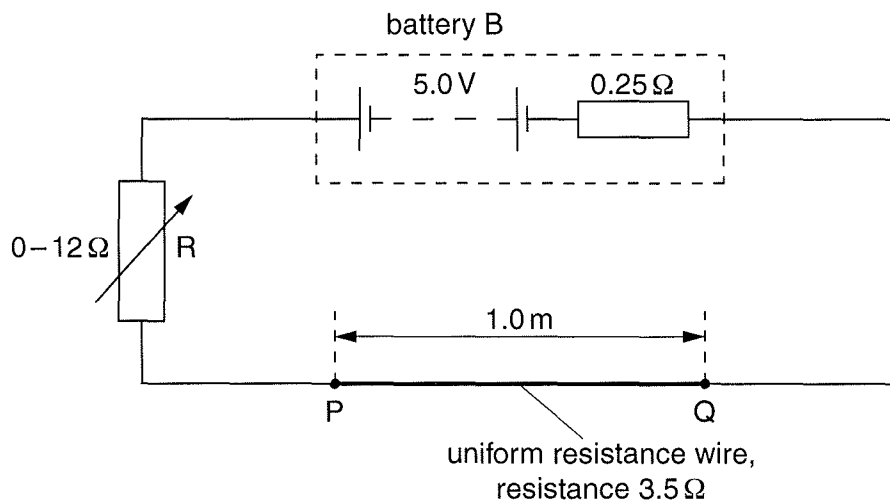


Fig. 3.1

Battery B has electromotive force (e.m.f.) 5.0V and internal resistance 0.25Ω. Wire PQ has length 1.0m and resistance 3.5Ω.

- (a) The resistance of R is varied from 0 to 12Ω.

Describe and explain the variation in the terminal potential difference (p.d.) across B. Numerical values are not required.

.....

.....

.....

.....

..... [3]

- (b) The resistance of R is set to 4.0Ω.

Calculate

- (i) the terminal p.d. across B,

p.d. = V [3]

(ii) the efficiency of power transfer of B.

efficiency = % [2]

(c) A cell C and a sensitive ammeter are connected to the circuit of Fig. 3.1, as shown in Fig. 3.2.

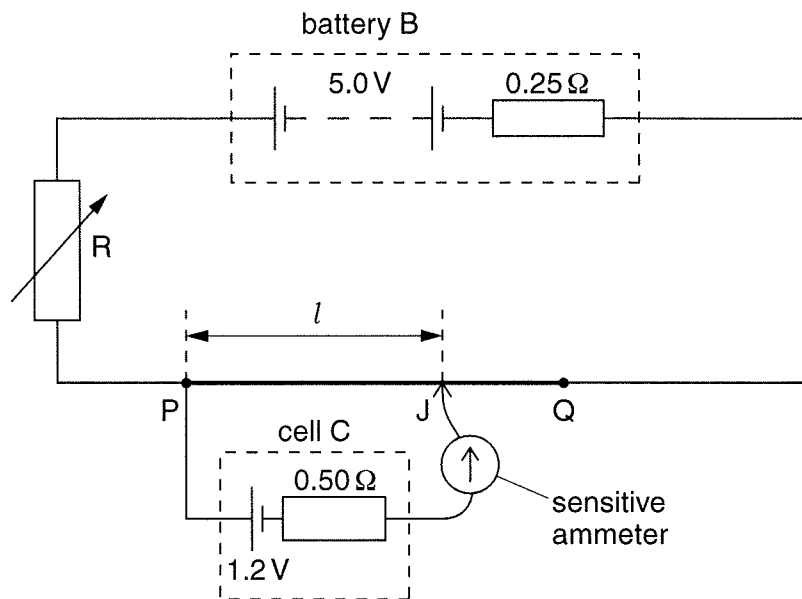


Fig. 3.2

Cell C has e.m.f. 1.2 V and internal resistance 0.50 Ω. The resistance of R remains at 4.0 Ω. The connection J is distance l from P.

The ammeter reads zero.

(i) State the value of the p.d. across PJ.

p.d. = V [1]

(ii) Calculate l .

l = m [2]

(iii) Explain why there is a reading on the ammeter when J is moved towards Q.

.....
 [1]

