

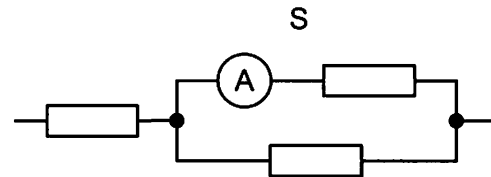
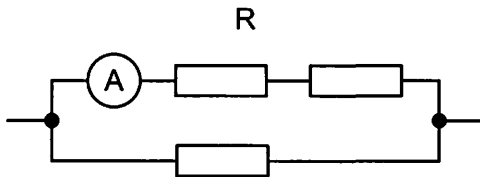


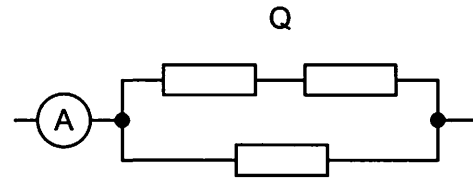- 24 Four different arrangements of identical resistors are connected to the same constant voltage power supply. An ammeter of negligible resistance is connected in each arrangement.



In which arrangement will the ammeter show the maximum reading and in which will it show the minimum reading?

	maximum ammeter reading	minimum ammeter reading
A	P	R
B	P	S
C	Q	R
D	Q	S

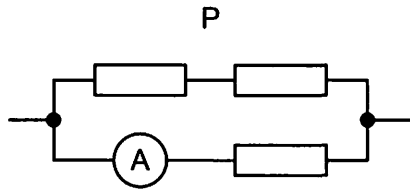