



- 8 (a) Distinguish between electrical resistance and resistivity.

resistance:

.....

resistivity:

.....

.....

[4]

- (b) An electric cable is made up of 24 thin strands of copper wire, as shown in Fig. 8.1.

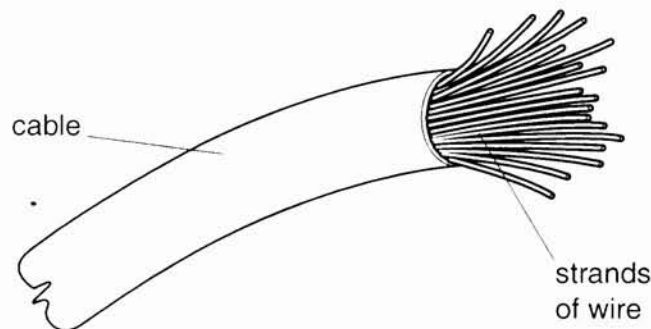


Fig. 8.1

Each strand has diameter 0.26 mm. Copper has resistivity $1.7 \times 10^{-8} \Omega \text{ m}$.

Calculate

- (i) the resistance of one strand of wire of length 1.0 m,

resistance = Ω [2]

- (ii) the resistance of the cable of length 5.0 m.

resistance = Ω [2]



- (c) A battery has an e.m.f. of 12.0 V and negligible internal resistance. A resistor of resistance $3.0\ \Omega$ is permanently connected to one of its terminals.

The battery and resistor form a power supply with terminals X and Y, as shown in Fig. 8.2.

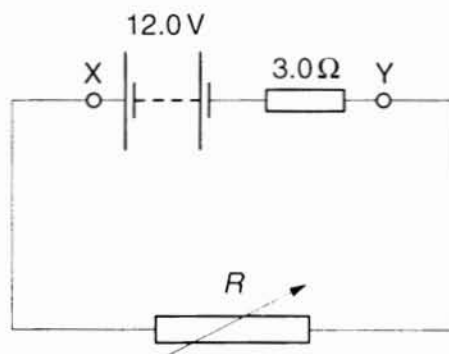


Fig. 8.2

A variable resistor of resistance R is connected across terminals X and Y.

- (i) Calculate

- the maximum possible current from the supply,

current = A [1]

- the minimum safe power rating of the $3.0\ \Omega$ resistor.

power = W [2]

- (ii) Suggest the purpose of the $3.0\ \Omega$ resistor.

.....
 [1]



- (d) The resistance R in the circuit of Fig. 8.2 is varied. The variation with R of the power P dissipated in the variable resistor is shown in Fig. 8.3.

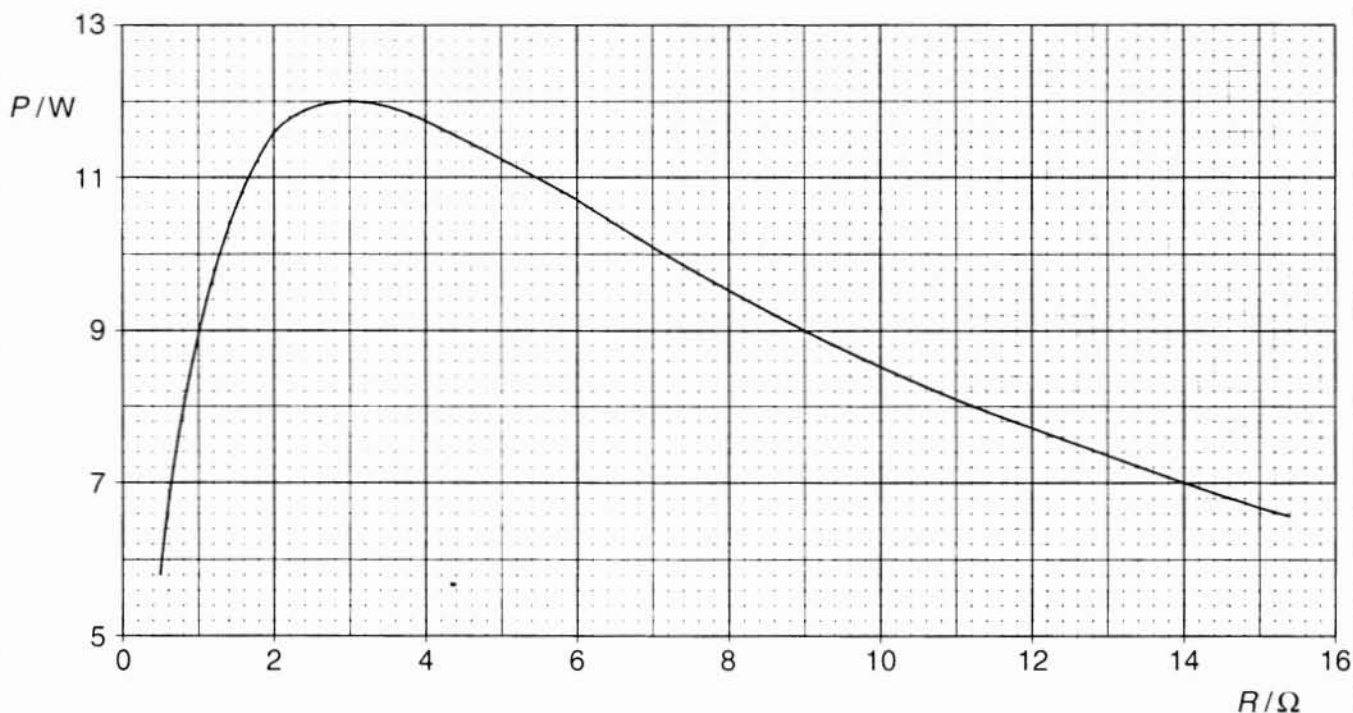


Fig. 8.3

- (i) State the two values of R at which the power dissipated in the variable resistor is 9.0W.

$R = \dots\dots\dots \Omega$ and $R = \dots\dots\dots \Omega$ [1]

- (ii) For each of the two values in (i), calculate the efficiency of transfer of power from the supply to the variable resistor.

$$\text{efficiency} = \left(\frac{\text{power output}}{\text{power supplied}} \right) \times 100\%$$

for resistance of $\dots\dots\dots \Omega$, efficiency = $\dots\dots\dots\%$

for resistance of $\dots\dots\dots \Omega$, efficiency = $\dots\dots\dots\%$

[5]



- (e) A battery is to be designed to provide the power for a component that has a fixed resistance.

The internal resistance r of the battery is to be chosen to provide maximum efficiency of energy transfer to the component.

Use your answers in (d) to state and explain the choice of r compared with the component's fixed resistance.

.....

.....

..... [2]