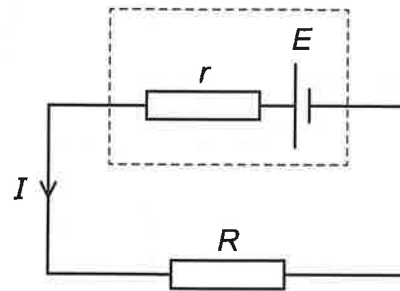


- 19 A cell of electromotive force (e.m.f.) E and internal resistance r is connected to a resistor of resistance R , as shown.



When $R = 4.0\ \Omega$ the current $I = 0.50\text{ A}$.

When $R = 10\ \Omega$ the current $I = 0.25\text{ A}$.

What are the e.m.f. E and the internal resistance r of the cell?

	e.m.f. E/V	internal resistance r/Ω
A	2.0	1.0
B	2.0	2.0
C	3.0	1.0
D	3.0	2.0

