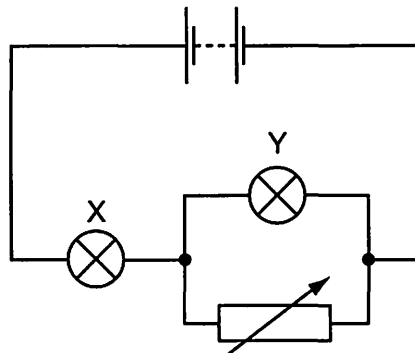


23 A circuit contains a battery, two identical lamps X and Y, and a variable resistor.



The resistance of the variable resistor is decreased.

What will happen to the brightness of the lamps?

	lamp X	lamp Y
A	brighter	brighter
B	brighter	less bright
C	less bright	brighter
D	less bright	less bright