

- 32** A sinusoidal alternating current has a peak value  $I_0$ .

Which expression is correct for the root-mean-square current  $I_{\text{rms}}$ ?

- A**  $I_{\text{rms}} = \frac{I_0}{2}$
- B**  $I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$
- C**  $I_{\text{rms}} = \sqrt{2}I_0$
- D**  $I_{\text{rms}} = 2I_0$

- 33** A 100% efficient transformer is connected as shown to a sinusoidal a.c. supply.