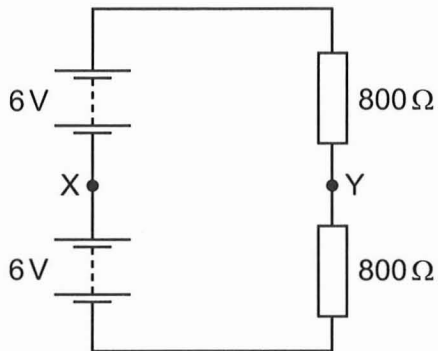


- 29 In the circuit shown, a wire of resistance 100Ω is used to make a connection between points X and Y.



What is the current in this wire?

- A 0 B 6.7 mA C 7.5 mA D 60 mA