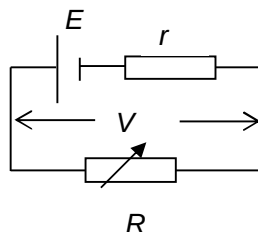


Answer: A


28



When $R = r$, $V = \frac{E}{2}$;

When $R = 4r$, $V' = \frac{4E}{5}$;

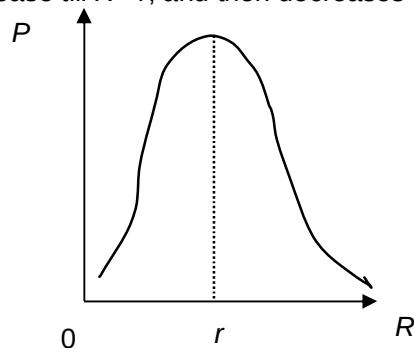Hence terminal pd increases. Power dissipated according to Maximum Power Theorem and thus it will increase till $R = r$, and then decreases as shown below.



Answer: C

29 energy supplied to wire in time $t = \frac{V^2 t}{R} = \frac{V^2 t}{\frac{R}{A}} = \frac{V^2 t A}{R}$