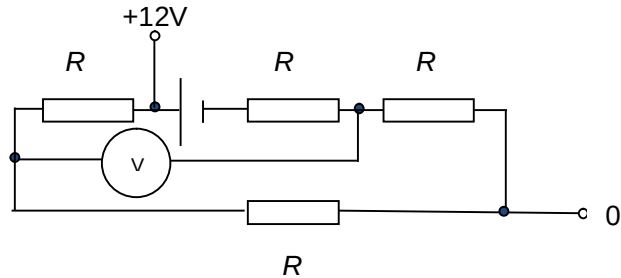


30



Pd across each resistor is 3 V. Pd across 2 resistors is 6 V but polarity is opposite. Hence voltmeter reading is zero.

Answer: A

31 A: S_1 , S_2 and S_3 closed: $R_{xy} = \frac{R}{2} + \frac{R}{2} = \frac{5R}{2}$