

Answer A

$$\begin{aligned} 26) \quad & (\text{emf}) = IR_1 + Ir_P \text{ ----- (1)} \\ & (\text{emf}) = IR_2 + Ir_Q \text{ ----- (2)} \end{aligned}$$

terminal potential difference = $\text{emf} - Ir$.
Since $r_P < r_Q$, terminal pd of P would be higher.

Output power = IV . Since both P and Q have the same current, higher V will give a higher power output, hence P has higher power output.

Answer A

$$27) \quad R = \rho l / A$$